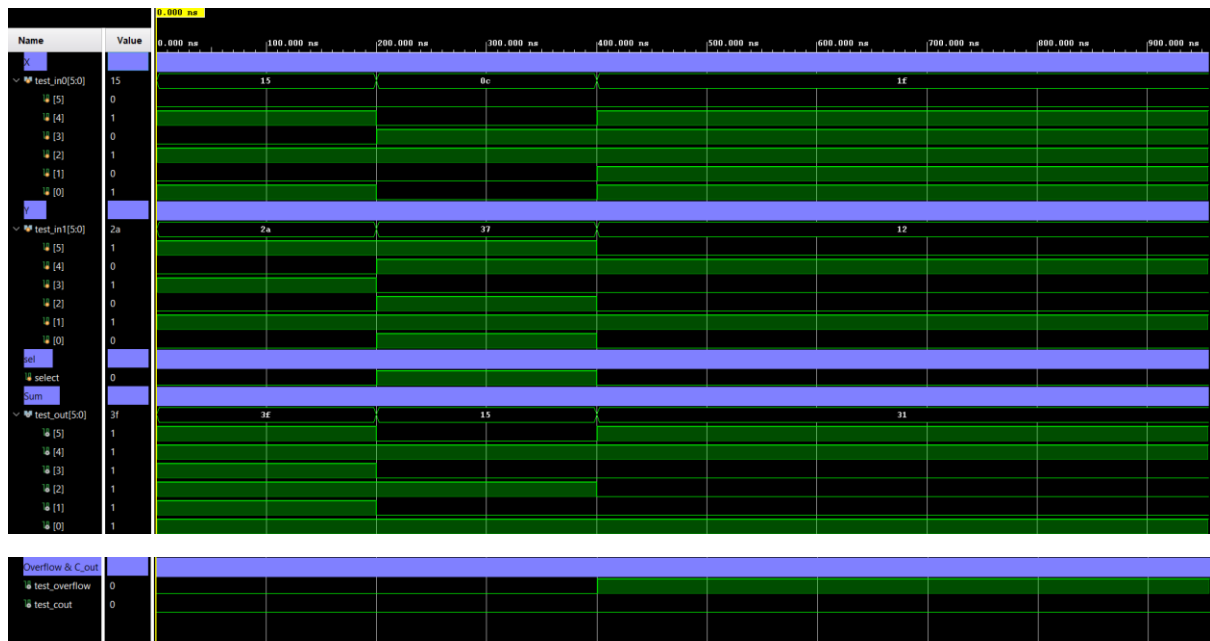



Test ID	x	y	sel	Cout (exp)	Overflow (exp)	Sum (exp)	Cout (obs)	Overflow (obs)	Sum (obs)	Pass/Fail
1	6'b010101	6'b101010	0	0	0	6'b111111	0	0	6'b111111	Pass
2	6'b001100	6'b110111	1	0	0	6'b010101	0	0	6'b010101	Pass
3*	-6'b100001	6'b010010	0	0	1	6'b110001	0	1	6'b110001	Pass
4	6'b111001	6'b100111	1	1	0	6'b010010	1	0	6'b010010	Pass
5*	6'b011011	-6'b101101	0	0	1	6'b101110	0	1	6'b101110	Pass
6	6'b110101	6'b011110	1	1	1	6'b010111	1	1	6'b010111	Pass
7	6'b111111	6'b111111	0	1	0	6'b111110	1	0	6'b111110	Pass
8	6'b000000	6'b000000	1	1	0	6'b000000	1	0	6'b000000	Pass
9	-6'b011010	-6'b101011	0	1	0	6'b111011	1	0	6'b111011	Pass

The circuit has passed all the tests as the observed output, overflow and sum values to what was expected. If I were to conduct this experiment again, I would increase the amount of test vectors with select as 1 in order to further verify the accuracy of the circuit when performing 2's complement subtraction.


Testbench Waveform[1-3]




Testbench Waveform[3-6]

 

Testbench Waveform[6-9]

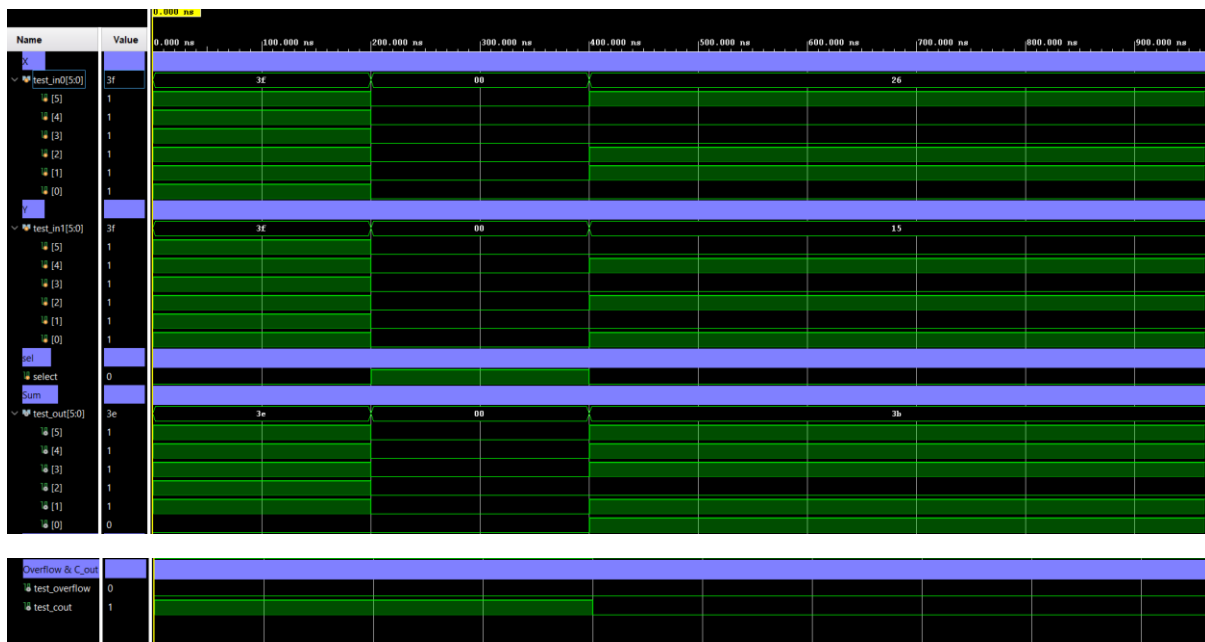

Block Diagram

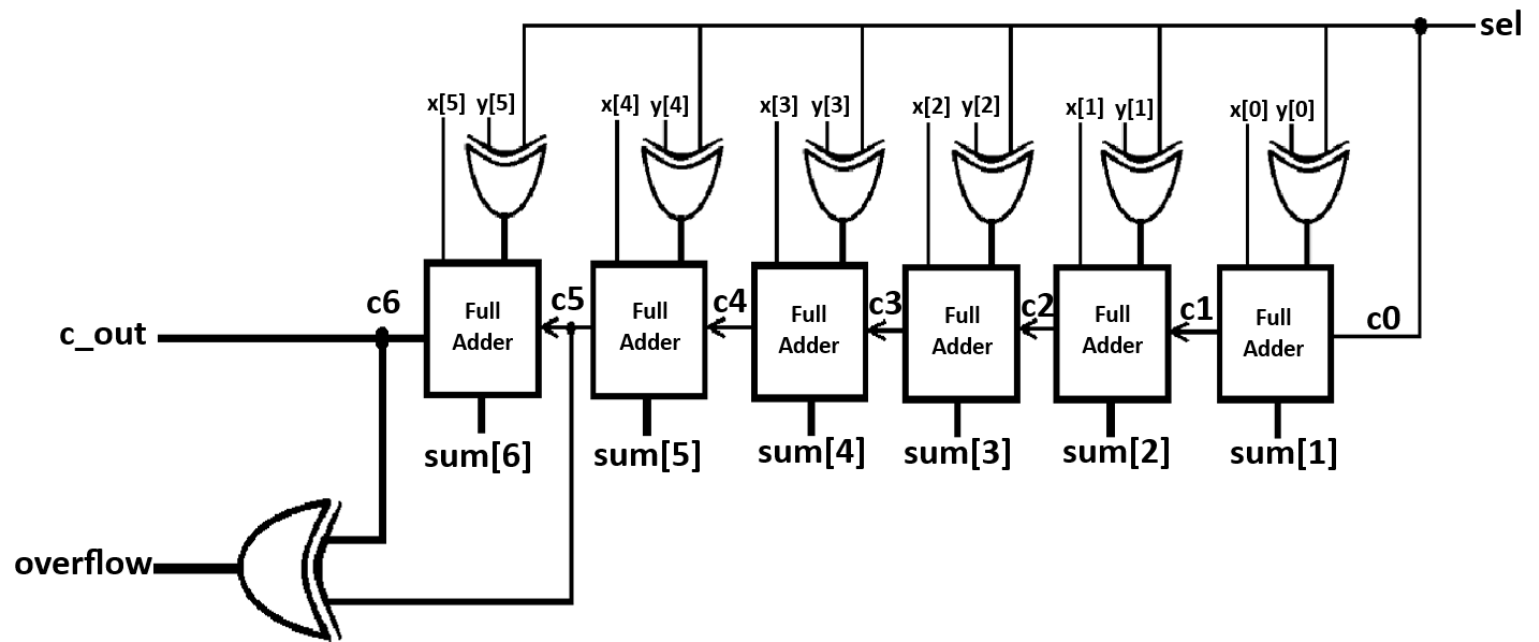

full_adder.v (from Blackboard)

```
module FullAdder(a, b, cin, s, cout);  
  
    // 3C7 LabD 2010  
  
    // a and b are the bits to add  
    // cin is carry in  
    input wire a, b, cin;  
  
    // s is the sum of a and b. cout is any carry out bit  
    // wires since just using assign here  
    output wire s, cout;  
  
    // logic for sum and carry  
    assign s = cin ^ a ^ b;  
    assign cout = (b & cin) | (a & cin) | (a & b);  
  
endmodule
```

6bit ripple adder.v

```
module sixbit_ripple_adder(
    input wire [5:0] x, y,          // 6-bit two's complement numbers to add
    input sel,                      // sel -> [0 = add] [1 = sub]
    output wire overflow,           // Output flagging overflow in the sum output
    [5:0] sum,                     // 2s complement sum of x and y
    c_out,                         // MSB Carry out from the sum
    wire c1, c2, c3, c4, c5, c6    // carry output for each full adder
);
    assign overflow = c6 ^ c5;      //overflow = c6 xor c5
    assign c0 = sel;               //initialise 1st output as the current value of sel
    FullAdder adder_1(.a(x[0]),.b(y[0] ^ sel), .cin(sel), .s(sum[0]), .cout(c1)); // 1st bit
    FullAdder adder_2(.a(x[1]),.b(y[1] ^ sel), .cin(c1), .s(sum[1]), .cout(c2)); // 2nd bit
    FullAdder adder_3(.a(x[2]),.b(y[2] ^ sel), .cin(c2), .s(sum[2]), .cout(c3)); // 3rd bit
    FullAdder adder_4(.a(x[3]),.b(y[3] ^ sel), .cin(c3), .s(sum[3]), .cout(c4)); // 4th bit
    FullAdder adder_5(.a(x[4]),.b(y[4] ^ sel), .cin(c4), .s(sum[4]), .cout(c5)); // 5th bit
    FullAdder adder_6(.a(x[5]),.b(y[5] ^ sel), .cin(c5), .s(sum[5]), .cout(c6)); // 6th bit
    assign c_out = c6;             // declare final carry output as output of ripple adder
endmodule
```

sbra_testbench.v (LabB - eq2 tb.v used as reference)

// Listing 1.7

// The `timescale directive specifies that

// the simulation time unit is 1 ns and

// the simulation timestep is 10 ps

`timescale 1 ns/10 ps

```
module sbra_testbench;
```

```
    // signal declaration
```

```
    reg [5:0] test_in0, test_in1;
```

```
    reg select;
```

```
    wire [5:0] test_out;
```

```
    wire test_overflow;
```

```
    wire test_cout;
```

```
    // instantiate the circuit under test
```

```
    sixbit_ripple_adder uut (.x(test_in0),.y(test_in1),.sum(test_out),.sel(select),.overflow(test_overflow),.c_out(test_cout));
```

```
// test vector generator

initial

begin

    //test vector 1

    test_in0 = 6'b010101;

    test_in1 = 6'b101010;

    select = 0;

    #200;

    // test vector 2

    test_in0 = 6'b001100;

    test_in1 = 6'b110111;

    select = 1;

    #200;

    // test vector 3

    test_in0 = -6'b100001;

    test_in1 = 6'b010010;

    select = 0;

    #200;

    //test vector 4

    test_in0 = 6'b111001;

    test_in1 = 6'b100111;

    select = 1;

    #200;

    // test vector 5

    test_in0 = 6'b011011;

    test_in1 = -6'b101101;

    select = 0;

    #200;

    // test vector 6

    test_in0 = 6'b110101;

    test_in1 = 6'b011110;

    select = 1;

    #200;

    // test vector 7

    test_in0 = 6'b111111;
```

```
test_in1 = 6'b111111;  
select = 0;  
  
#200;  
  
// test vector 8  
test_in0 = 6'b000000;  
test_in1 = 6'b000000;  
select = 1;  
  
#200;  
  
// test vector 9  
test_in0 = -6'b011010;  
test_in1 = -6'b101011;  
select = 0;  
  
#200;  
  
// stop simulation  
//$stop;  
  
end  
  
endmodule
```