
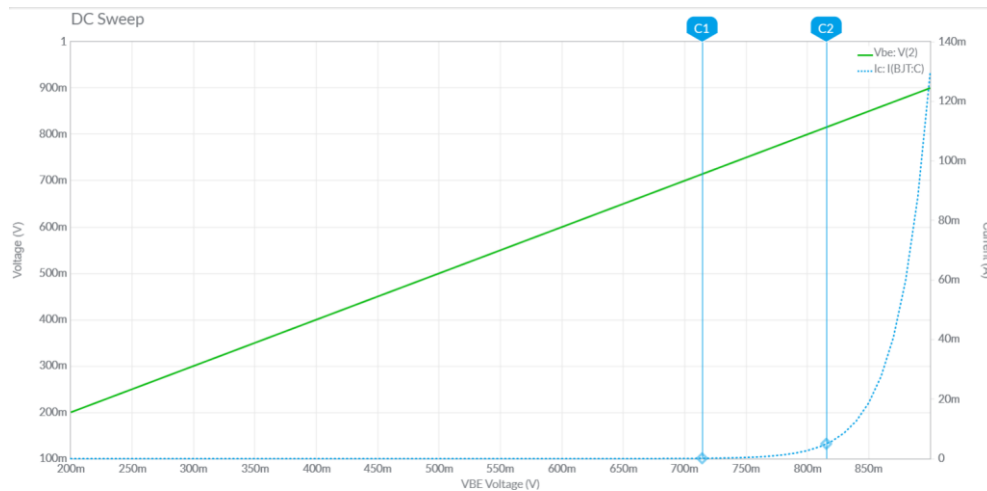


## 3C2 - Simulation Lab

Stephen Komolafe (21336975)

### Bipolar Junction Transistor Current-Voltage Characteristic

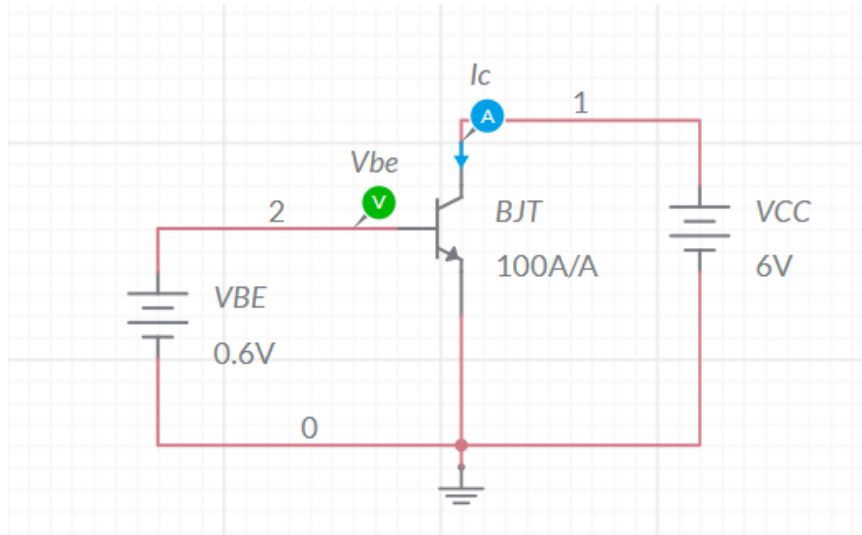1. Plot the collector current ( $I_C$ ) against the base-emitter voltage ( $V_{BE}$ ).




2. Find the two voltages:

$$V_{BE}^{cut\ in} (@100.00\ \mu\text{A}) = 714.18\text{ mV}$$

$$V_{BE}^{on} (@5.00\text{ mA}) = 815.36\text{ mV}$$



## Transistor Characteristics

1. Plot  $I_D$  against  $V_{DD}$ .

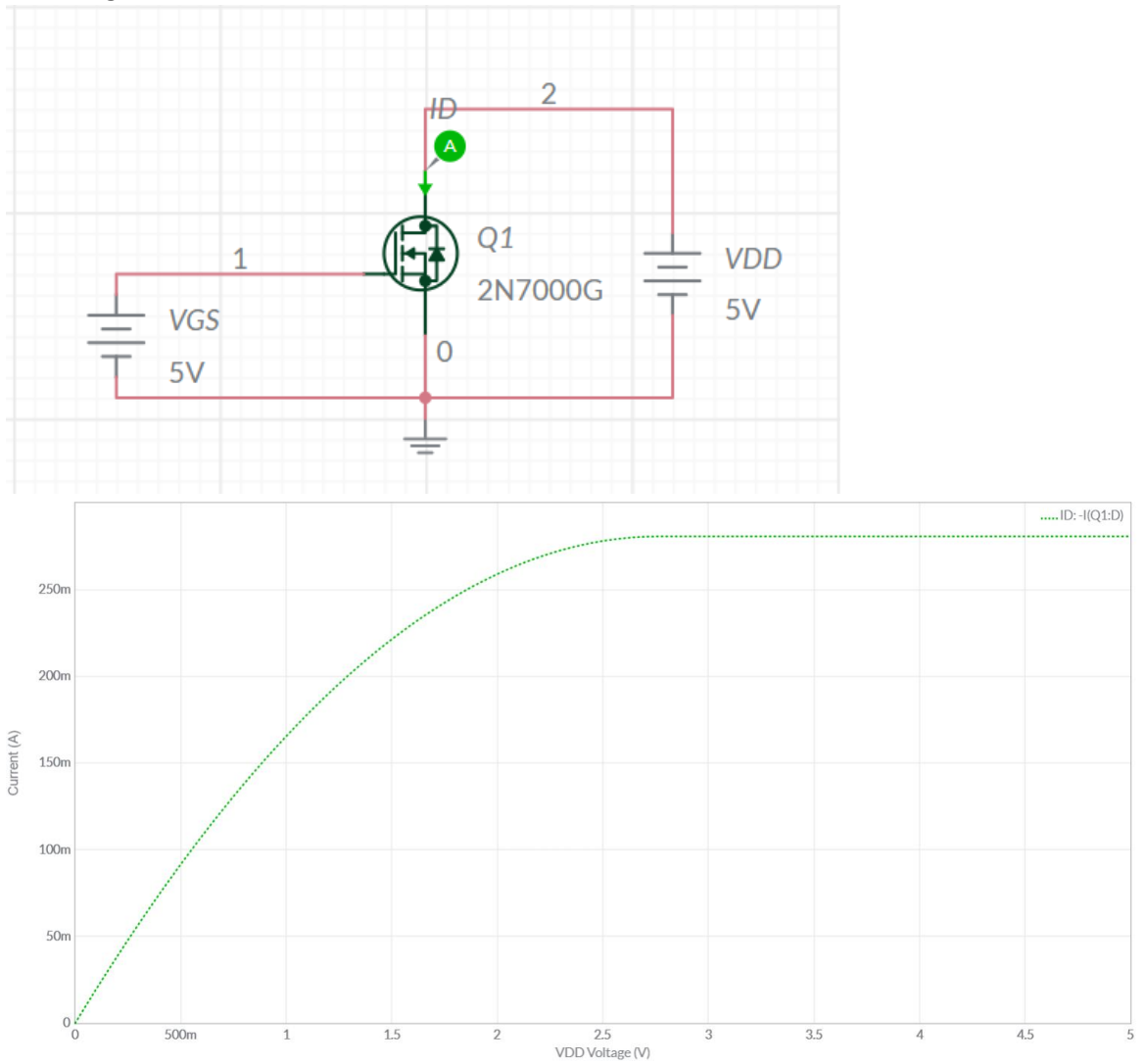

## Resistor Load Inverters

### -NMOS Inverter

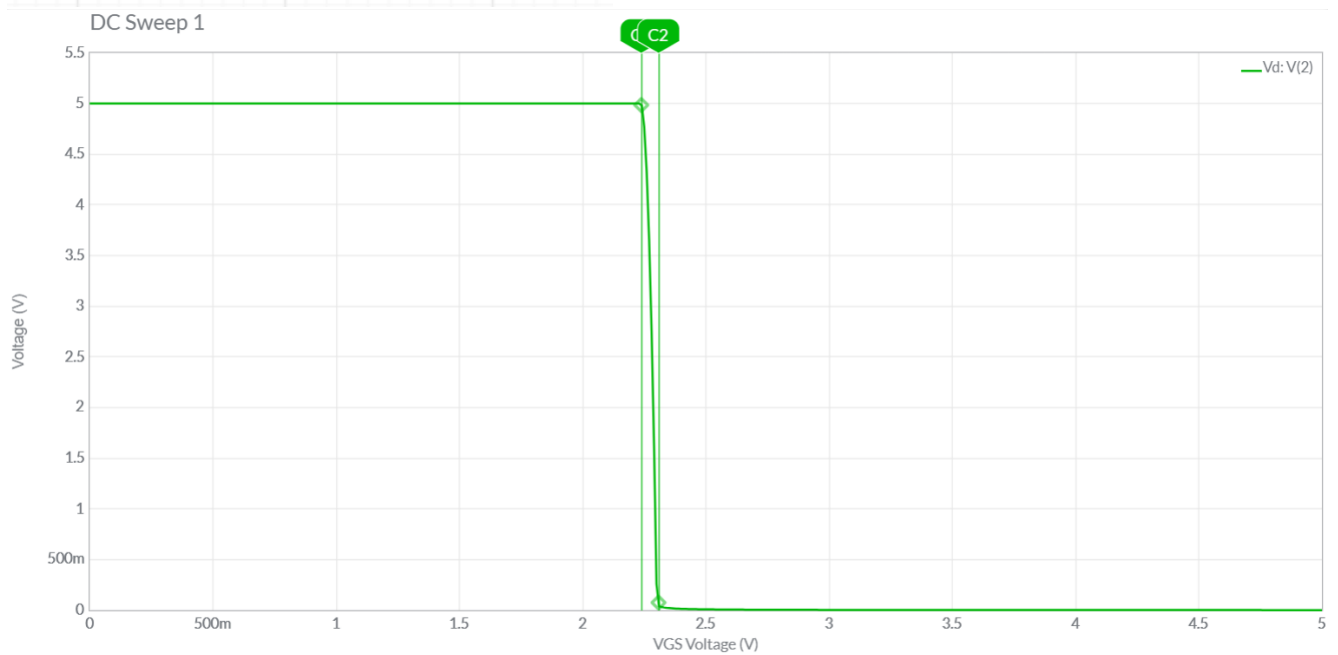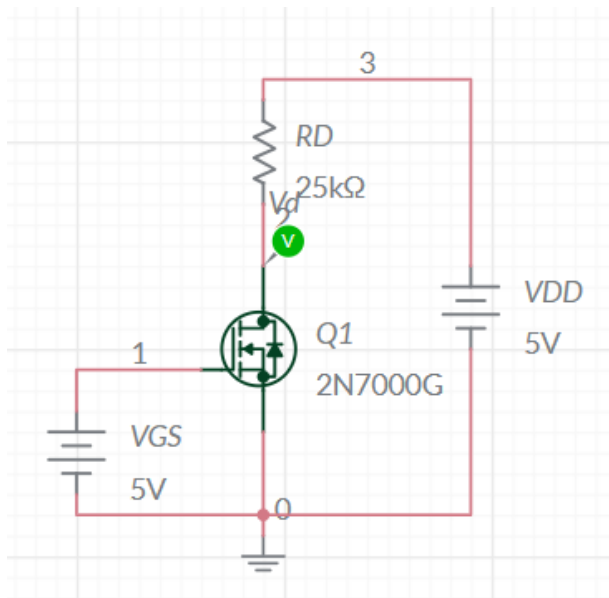

1. Are the outputs as expected?

“For  $V_{GS} < V_T$ ,  $V_O$  should be  $V_{DD}$ ”

- While  $V_{GS}$  is at 0V,  $V_O$  (represented by the y-axis) remains at 5V, and is equal to  $V_{DD}$  as expected.

“

”

For  $V_{GS} = V_{DD}$ ,  $V_O$  should be

$$(V_{DD} - V_T + \frac{1}{kR_D}) \pm \sqrt{(V_{DD} - V_T + \frac{1}{kR_D})^2 - \frac{2V_{DD}}{kR_D}}$$

$$V_{DD} = 5V$$

$$V_{GS} = 5V$$

$$R_D = 25k\Omega$$

$$k = g_{fs}(\text{datasheet}(1)) = 0.6$$

$$V_T \approx 2.2299V(\text{approx. from graph})$$

$$V_O \approx \left(5 - 2.2299 + \frac{1}{(0.6)(25000)}\right) \pm \sqrt{\left(5 - 2.2299 + \frac{1}{(0.6)(25000)}\right)^2 - \frac{2(5)}{(0.6)(25000)}}$$

$$\approx 2.770166 \pm 2.770046$$

$$\therefore V_O \approx 2.77V \pm 2.77V$$

#### Voltage Levels (Measured using cursors)

$$V_{IL} = 2.2395V$$

$$V_{IH} = 2.31V$$

$$V_{OL} = 39.838 mV$$

$$V_{OH} = 4.9823V$$

#### Voltage Levels (Theoretical)

$$V_{IL} = V_T + \frac{1}{2(K_n)(R_D)}$$

$$\approx 2.2299 + \frac{1}{2(0.6)(25000)}$$

$$\approx 2.229933$$

$$\therefore V_{IL} \approx 2.229V$$

$$V_{IH} = V_T + 2\sqrt{\frac{V_{DD}}{3(K_n)(R_D)}} - \frac{1}{2(K_n)(R_D)}$$

$$\approx 2.2299 + 2\sqrt{\frac{5}{3(0.6)(25000)}} - \frac{1}{2(0.6)(25000)}$$

$$\approx 2.25094$$

$$\therefore V_{IH} \approx 2.25V$$

$$V_{OL} = \sqrt{\frac{V_{DD}}{3(K_n)(R_D)}}$$

$$= \sqrt{\frac{5}{3(0.6)(25000)}}$$

$$= 0.0105V$$

$$\therefore V_{OL} = 10.5mV$$

$$V_{OH} = V_{DD} - \frac{1}{4(K_n)(R_D)}$$



$$= 5 - \frac{1}{4(0.6)(25000)}$$

$$= 4.99998$$

$$\therefore V_{OH} = 4.99V$$

The voltage levels found using the cursors roughly match the values derived using the theoretical methods

### - NPN BJT Inverter

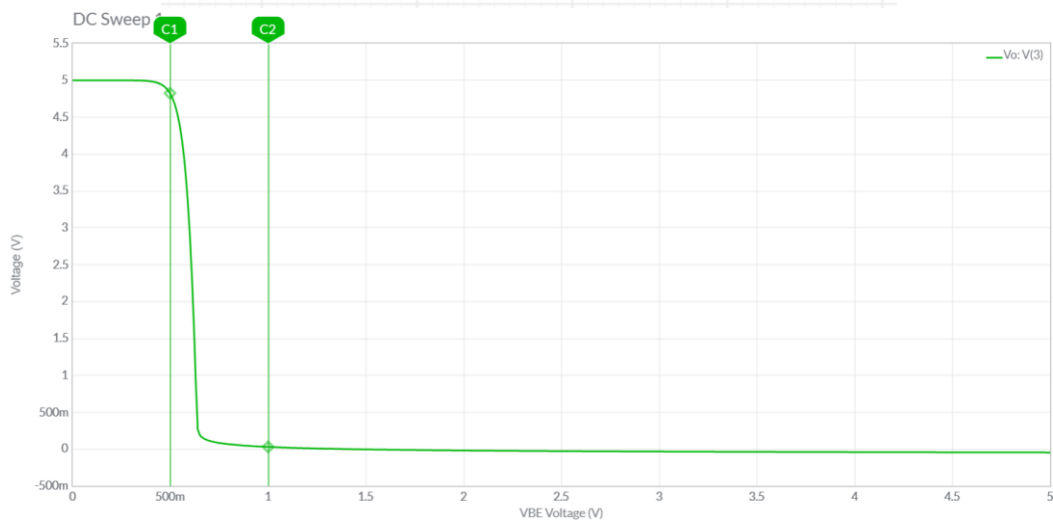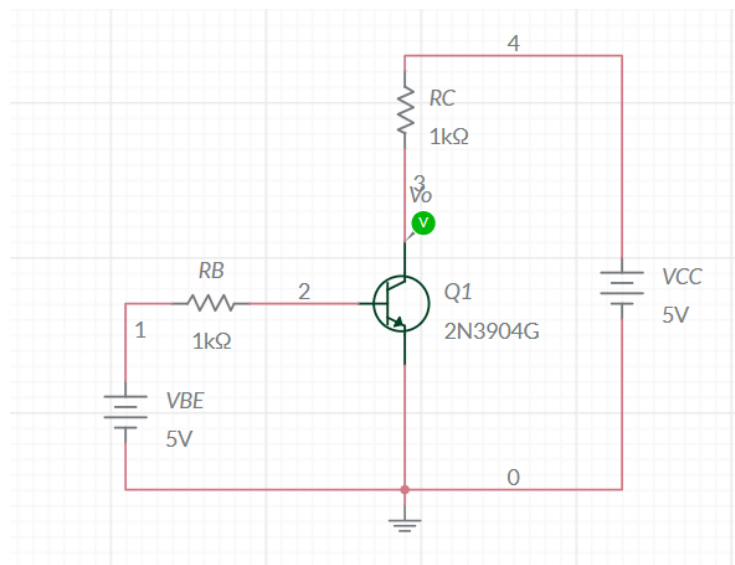

### Critical Voltages (Measured using cursors)

$$V_{IL} = 497.8mV$$

$$V_{IH} = 1V$$

$$V_{OL} = 29.917mV$$

$$V_{OH} = 4.8157V$$

### Critical Voltages (Circuit Theory)

$$V_{BE} = 5V \quad V_{CC} = 5V \quad R_B, R_C = 1k\Omega \quad B_f = h_{FE}(\text{datasheet}(2)) = 300$$

$$V_{IL}^{MAX} = V_{BE}^{CUT-IN} \sim 0.6V \text{ (L10: BJT Applications)}$$

$$V_{IH}^{MIN} = V_{BE}^{SAT} + \frac{R_B}{\beta_F R_C} (V_{CC} - V_{CE}^{SAT})$$

$$V_{BE}^{SAT} \sim 0.8V \text{ (L10: BJT Applications)}$$

$$V_{CE}^{SAT} \sim 0.2V \text{ (datasheet}(2))$$

$$V_{IH}^{MIN} = 0.8 + \frac{1000}{(300)(1000)} (5 - 0.2)$$

$$\therefore V_{IH}^{MIN} = 0.816V$$

$$V_{OL} = V_{CE}^{SAT} \text{ (L10: BJT Applications)}$$


$$\therefore V_{OL} = 0.2V$$

$$V_{OH} = V_{CC} \text{ (L10: BJT Applications)}$$



$$\therefore V_{OH} = 5V$$

---

$$@R_C = 4k\Omega$$

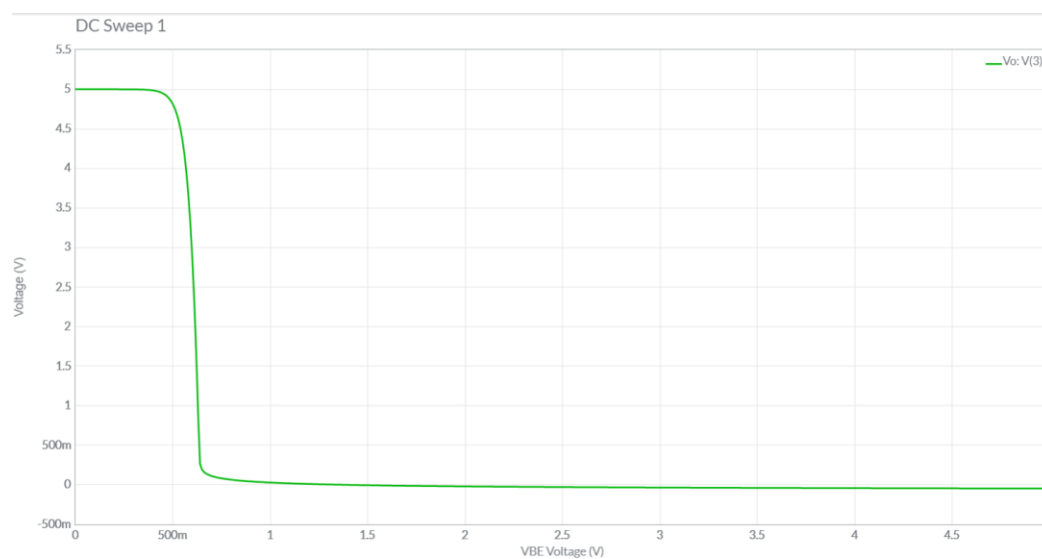

## CMOS Inverter

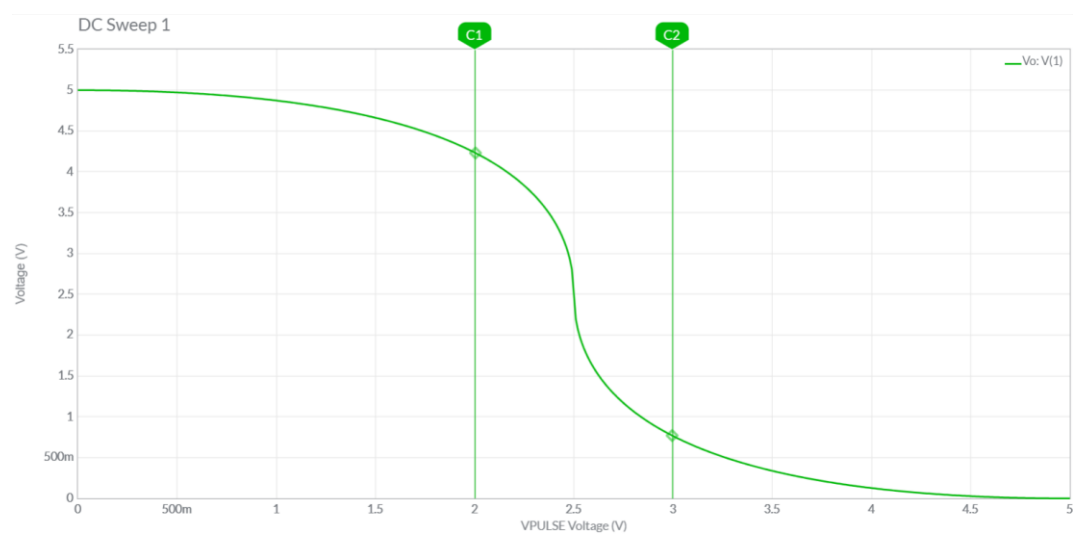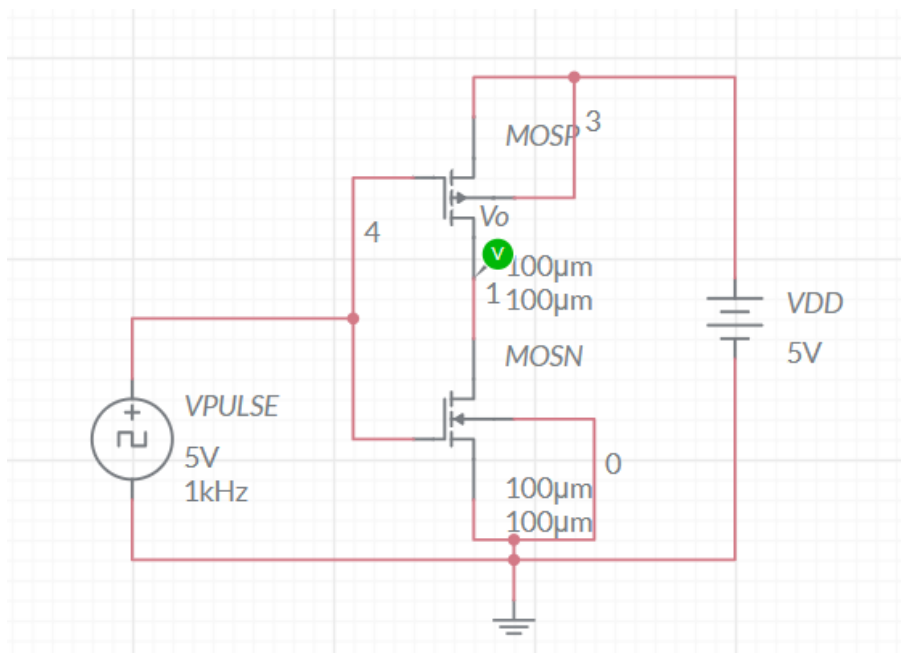

### Critical Voltages (Measured using cursors)


$$V_{IL} = 2.0044V$$

$$V_{IH} = 2.9956V$$


$$V_{OL} = 769.43mV$$

$$V_{OH} = 4.2306V$$

## CMOS NAND Gate

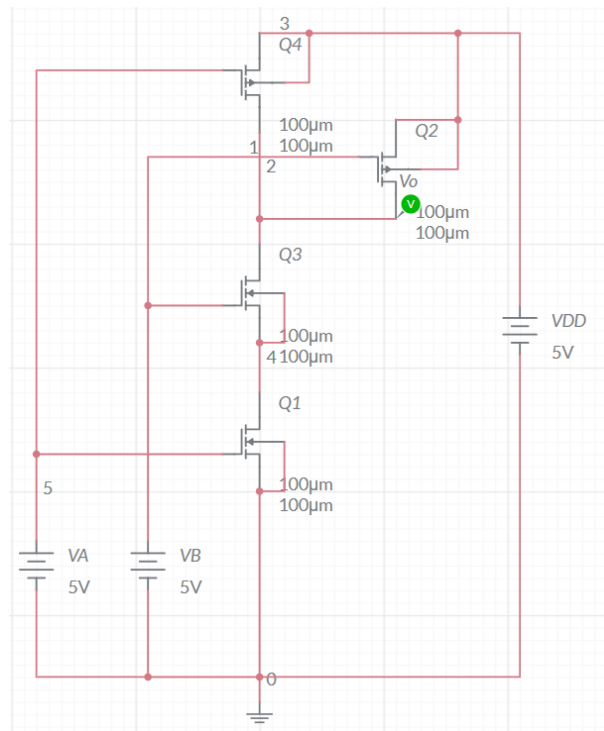


- VB with VA = 5 V, plot VO against VB

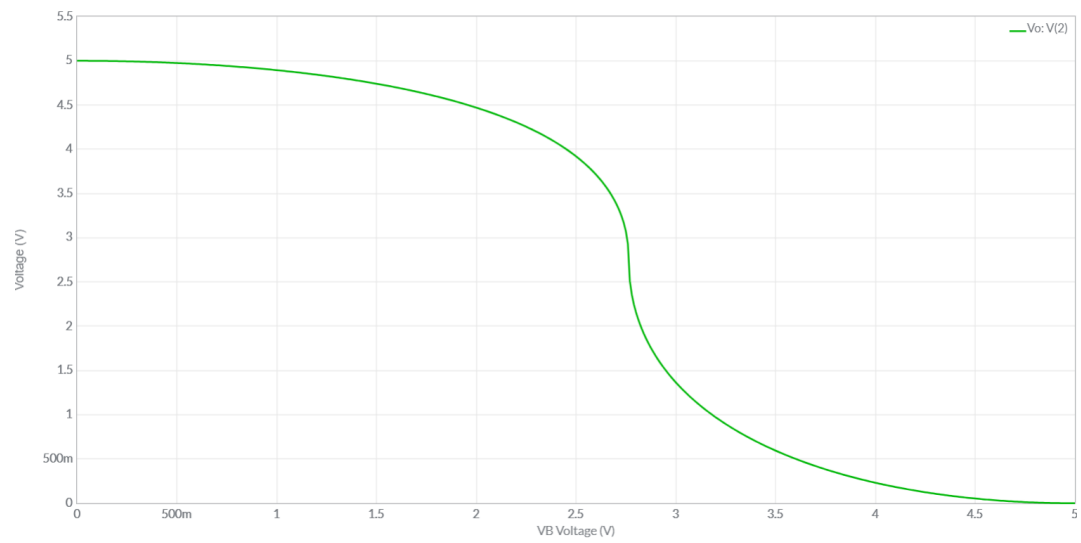



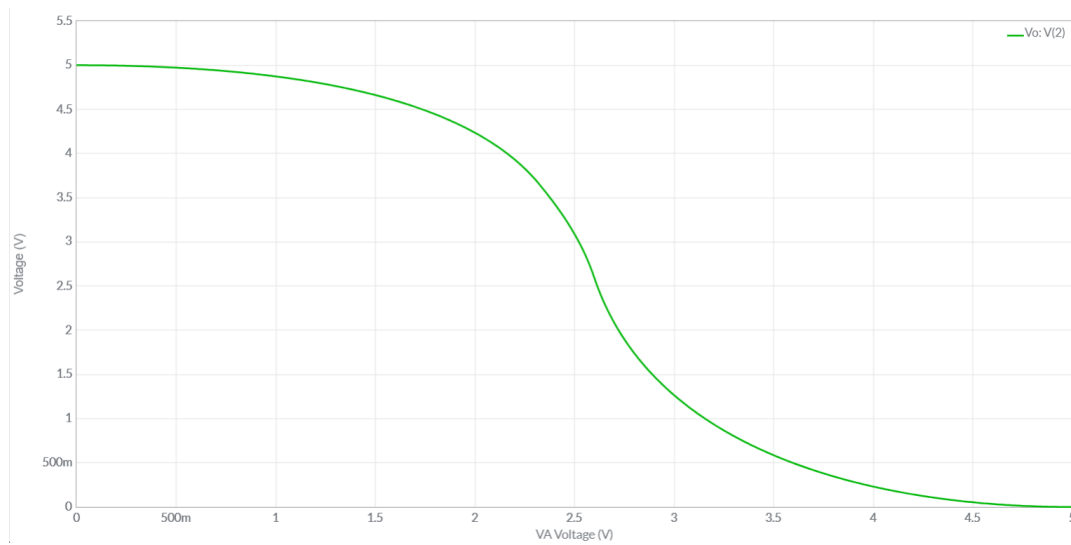- VA with  $V_B = 5\text{ V}$ , plot  $V_O$  against  $V_A$



The decline of the output voltage is more gradual in the  $V_O/V_A$  plot compared to the  $V_O/V_B$  plot, where the output sharply decreases when  $V_B$  is within the range of 2.72V to 2.82V.

## Datasheets

### (2N7000)

1. <https://www.st.com/resource/en/datasheet/cd00005134.pdf>

### (2N3904)

2. <https://www.onsemi.com/pdf/datasheet/2n3904-d.pdf>